

Impedance Terminations

What's the Value

Douglas Brooks

There is a lot of confusion in the industry about “differential impedance.” I wrote a column last August¹ specifically on this topic. In hindsight I can see that the article may have been too specific, because it looked specifically at differential impedance, and not at impedance in general. The article pointed out that in the case of differential signals, a transmission line terminating resistor needs to be adjusted by a correction factor related to the coupling between two traces. But in fact, **IT IS ALWAYS TRUE** that the proper terminating resistor for a transmission line needs to be adjusted for adjacent trace coupling! Here's why:

Figure 1 illustrates a typical (transmission line) trace with voltage V_1 , impedance Z_0 and current i . Figure 1 (b) illustrates the general case of two traces fairly close together. By convention we call the intrinsic impedance of trace 1 Z_{11} (instead of Z_0) and that for trace 2 Z_{22} . The coupling coefficient between the traces is k , so the induced current from trace 2 into trace 1 has a magnitude $k \cdot i_2$. Thus the total current on trace 1 is $i_1 + k \cdot i_2$. Now here's the bad news: The voltage at any place on Trace 1 is:

$$V_1 = i_1 \cdot Z_{11} + k \cdot i_2 \cdot Z_{11}$$

Therefore, the impedance on trace 1 **at any point** is:

$$V_1 / i_1 = Z_{11} + Z_{11} \cdot k \cdot i_2 / i_1 \quad \text{Eq. 1}$$

Lets define a term $Z_{12} = Z_{11} \cdot k \cdot i_2 / i_1$. This is that portion of the impedance of trace 1 caused by mutual coupling from trace 2. When we do this, we get the impedance along trace 1 as

$$V_1 / i_1 = Z_{11} + Z_{12} \quad \text{Eq. 2}$$

You will find this equation in almost all textbooks that discuss signal networks and generalized signal analyses. Eq. 2 can be generalized for any number of traces and is often expressed in matrix algebra form. These kinds of signal analysis problems are usually solved using matrix algebra.

Since this is the impedance along Trace 1 **at any point**, it is also the impedance at the end point. It is, therefore, the proper terminating impedance for the trace. Therefore, **all** transmission lines need to be terminated, **not** in their characteristic impedance Z_0 , but in a terminating resistance Z_0 **adjusted for** this coupling impedance. That's the bad news.

Now what are the practical implications for this? Let's look at several cases.

- If trace 2 is far away, then k is very small. In this case, Z_{12} is negligible and is ignored.
- If i_2 is zero then Z_{12} is zero and has no effect.
- If i_2 is very small compared to i_1 , then Z_{12} is very small and can be ignored.

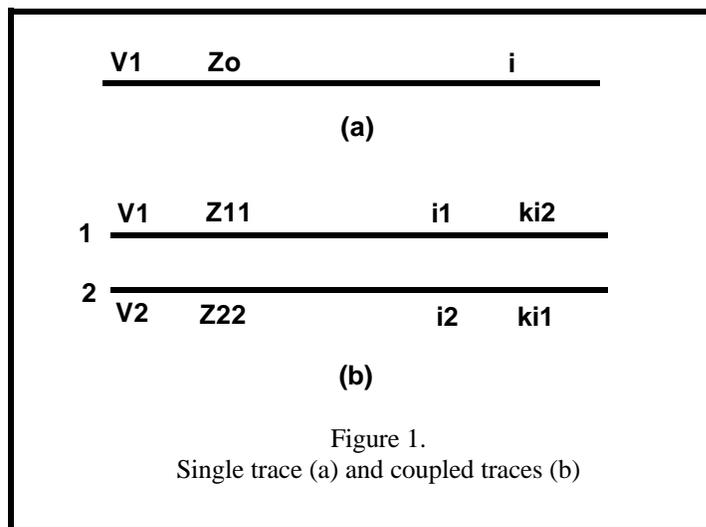


Figure 1.
Single trace (a) and coupled traces (b)

- If i_2 is constant, then k is zero – only **changing** currents couple into adjacent traces.

So far, even though it is true that the terminating resistor must be adjusted for Z_{12} , the adjustment is zero or negligible and is ignored. But here is a more troubling case. What if trace 2 is close to trace 1, carries a significant current, and that current is totally uncorrelated with i_1 ? By uncorrelated I mean there is no relationship whatever between the two currents. This is typical for most cases where signal buses route close together across a board. For the purposes here lets think of current i_2 as being purely random in nature.

In this case we **would** adjust for Z_{12} if we could. But Z_{12} is a random variable and is constantly changing. Therefore, what value do we use? Well the **average** value of Z_{12} is zero, so we do not adjust for it and we continue to use simply Z_0 as the best choice for the terminating resistor. That doesn't mean that there won't be noise on Trace 1 caused by this coupled current. There most certainly will be. In fact we know that noise as crosstalk!

So, even though it is true that we should always adjust trace terminations to correct for adjacent trace coupling, it turns out that in almost every case the correct adjustment is zero. That's the good news. And that's why we rarely see this discussed.

Now, let's take a very special case. Suppose current i_2 is **exactly** correlated with i_1 . Then, at least conceptually, we know exactly what Z_{12} is and we should always adjust for it. The adjustment may be plus or minus, depending on the correlation.

When is i_2 correlated with i_1 ? In the case of differential signals, i_2 is exactly $-i_1$ (minus i_1) and in the case of common mode signals i_2 is exactly equal to i_1 . So for differential signals the proper trace termination is $Z_{11}-Z_{12}$ and for common mode signals the proper termination is $Z_{11}+Z_{12}$. It is easy to say this. It is a little more difficult to actually calculate it! I discuss the calculation issues in the previous article.

Now, many of us have seen the expression that differential impedance is $2*(Z_{11}-Z_{12})$. Where does the factor 2 come from? Well, the proper termination for **each** trace is $Z_{11}-Z_{12}$. That is the case if we were terminating to ground (half way between V_1 and V_2). But if i_1 equals $-i_2$ and if both terminating resistors were connected to ground, there would be no net current through ground. Every increment of current through R_1 would return through R_2 . So why connect

them to ground? There is no benefit to connecting them to ground, since ground is not needed at all. And there is one big disadvantage to connecting them to ground. Even the best ground has some noise on it. Why would you connect a noise source (ground) to your signals if you didn't need to? The answer is that you most assuredly would not. What you would do is connect Trace 1 directly to Trace 2. The correct value for this termination would be $R_1 + R_2$ or $2*R_1$ or $2*(Z_{11}-Z_{12})$. That's where the differential impedance formula comes from!

The case for common mode signals differs in only two respects. The sign of Z_{12} is changed, so the correct termination is $Z_{11}+Z_{12}$, and the common mode termination impedance is calculated as $(Z_{11}+Z_{12})/2$. This is because both terminating resistors **do** connect to ground in the common mode case, so they appear to the circuit as a pair of parallel resistors. Therefore, the common mode impedance is expressed as the parallel equivalent of the two terminations.

Footnotes

1. "Differential Impedance, What's the Difference", PC Design, August, 1998, p.34